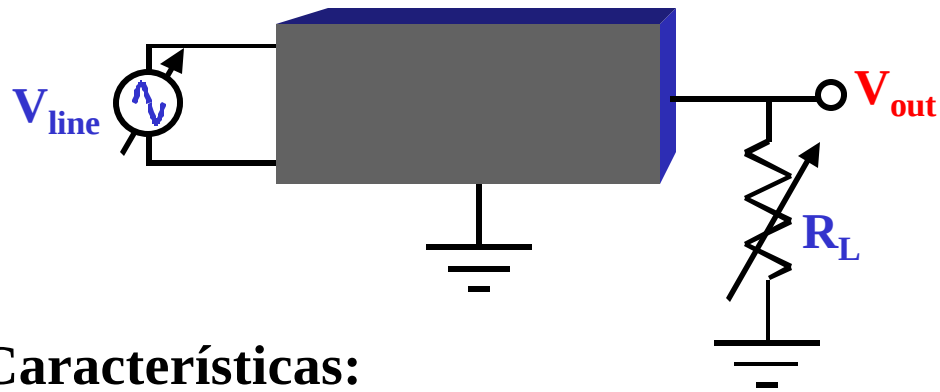


Fuentes de alimentación reguladas




Características:

$$\text{Load regulation} = \frac{V_{NL} - V_{FL}}{V_{FL}} \times 100\%$$


$$\text{Line regulation} = \frac{V_{HL} - V_{LL}}{V_{LL}} \times 100\%$$

$$R_{TH} = \frac{V_{NL} - V_{FL}}{I_{FL}}$$

Reguladores paralelos – Diodo Zener

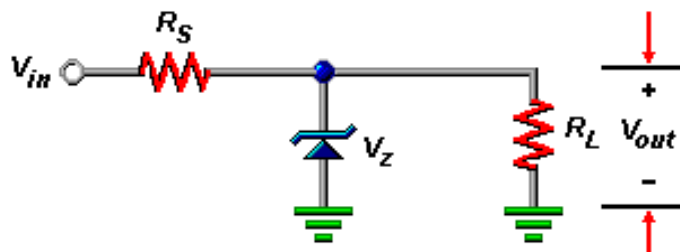

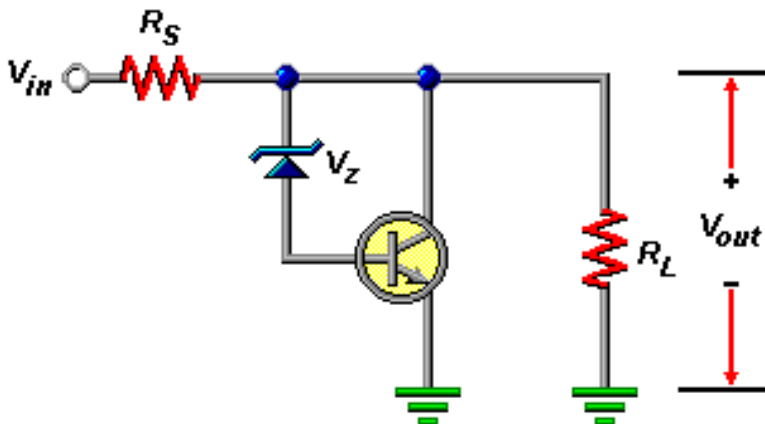
$$\begin{aligned} V_{out} &= V_Z \\ I_S &= \frac{V_{in} - V_{out}}{R_S} \\ I_L &= \frac{V_{out}}{R_L} \\ I_Z &= I_S - I_L \end{aligned}$$



$$\begin{aligned} V_{out} &= V_Z + V_{BE} \\ I_S &= \frac{V_{in} - V_{out}}{R_S} \\ I_L &= \frac{V_{out}}{R_L} \\ I_C &\cong I_S - I_L \end{aligned}$$

Reguladores paralelos – Diodo Zener

Tensión de salida mayor que V_Z

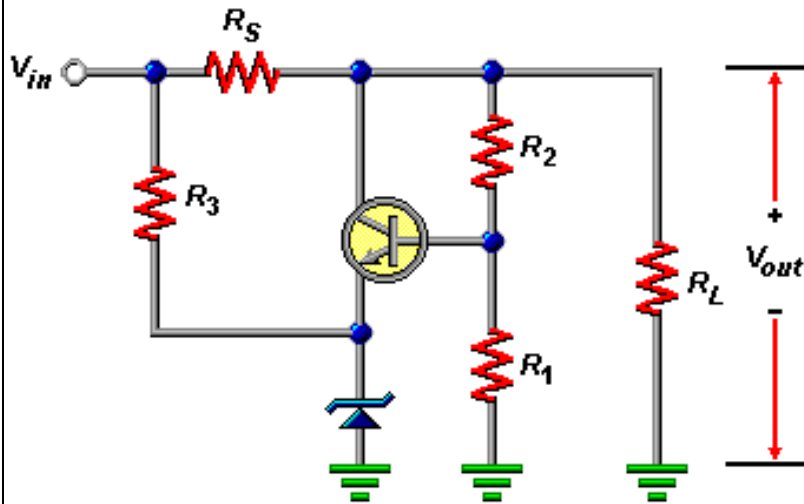

$$V_{out} \cong \frac{R_1 + R_2}{R_1} (V_Z + V_{BE})$$


$$I_S = \frac{V_{in} - V_{out}}{R_S}$$

$$I_L = \frac{V_{out}}{R_L}$$

$$I_C \cong I_S - I_L$$

Reguladores paralelos – Diodo Zener

Regulación mejorada

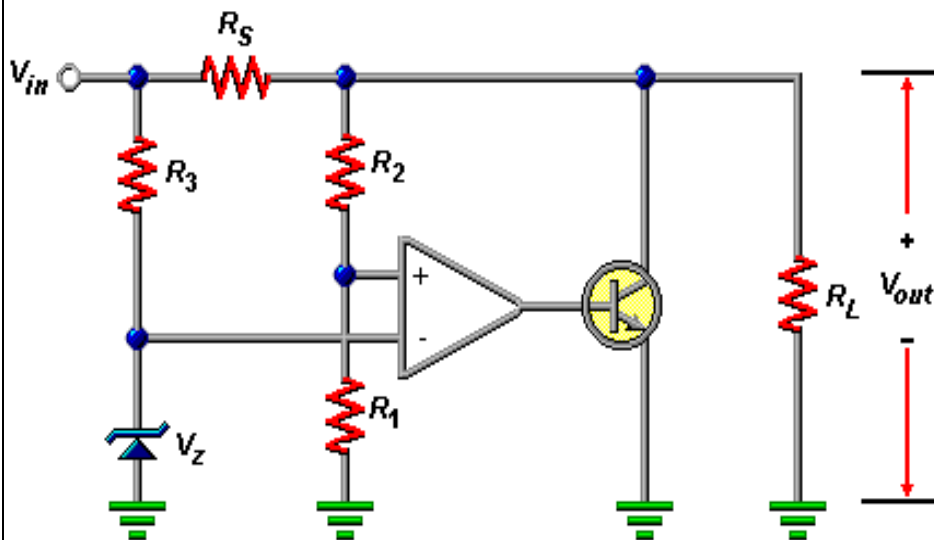


$$V_{out} = \frac{R_1 + R_2}{R_1} V_Z$$

$$I_S = \frac{V_{in} - V_{out}}{R_S}$$

$$I_L = \frac{V_{out}}{R_L}$$


$$I_C \cong I_S - I_L$$

Regulador serie – Seguidor de zener

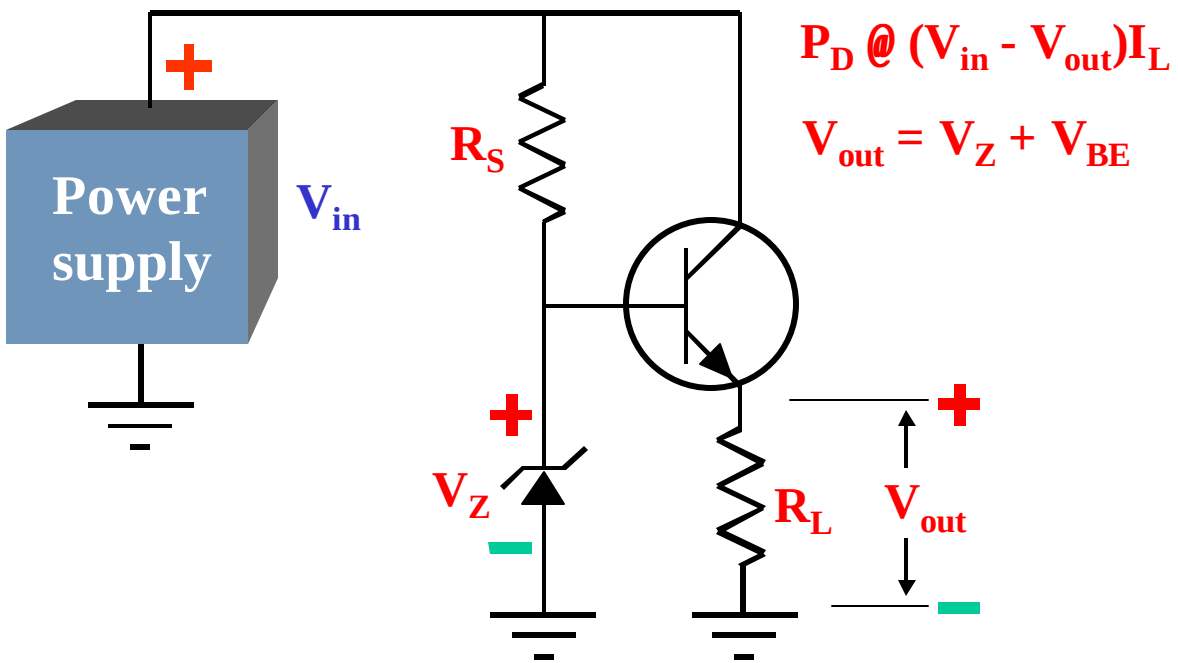


Regulador serie con dos transistores
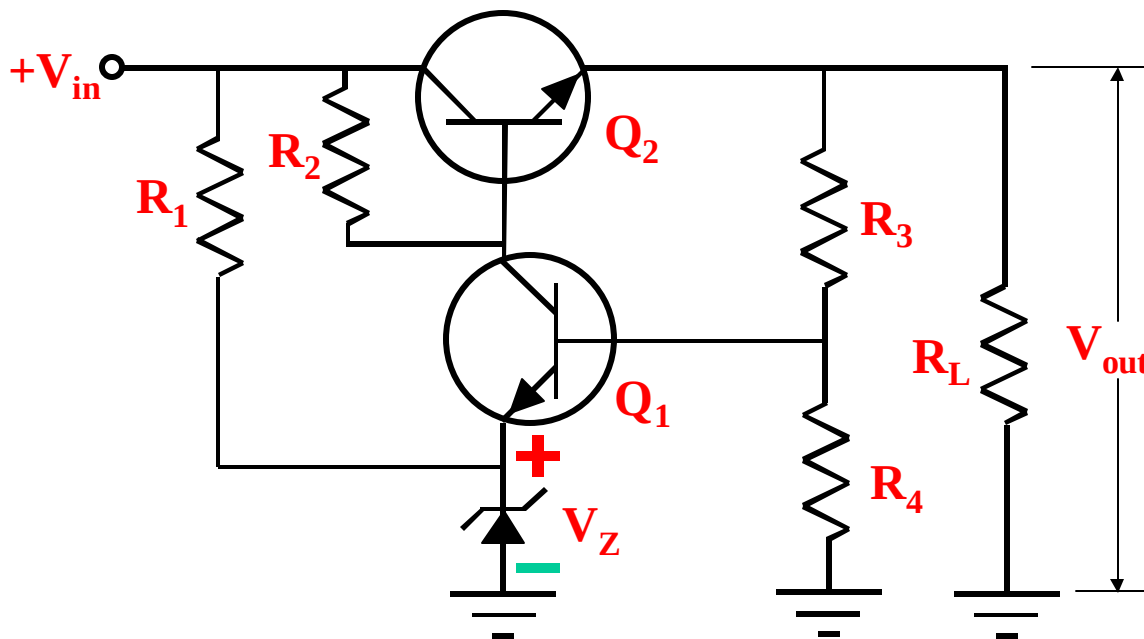
$$V_{out} = \frac{R_3 + R_4}{R_4} (V_Z + V_{BE})$$



Regulador serie mejorado

$$V_{out} = \frac{R_2 + R_3}{R_3} V_Z$$

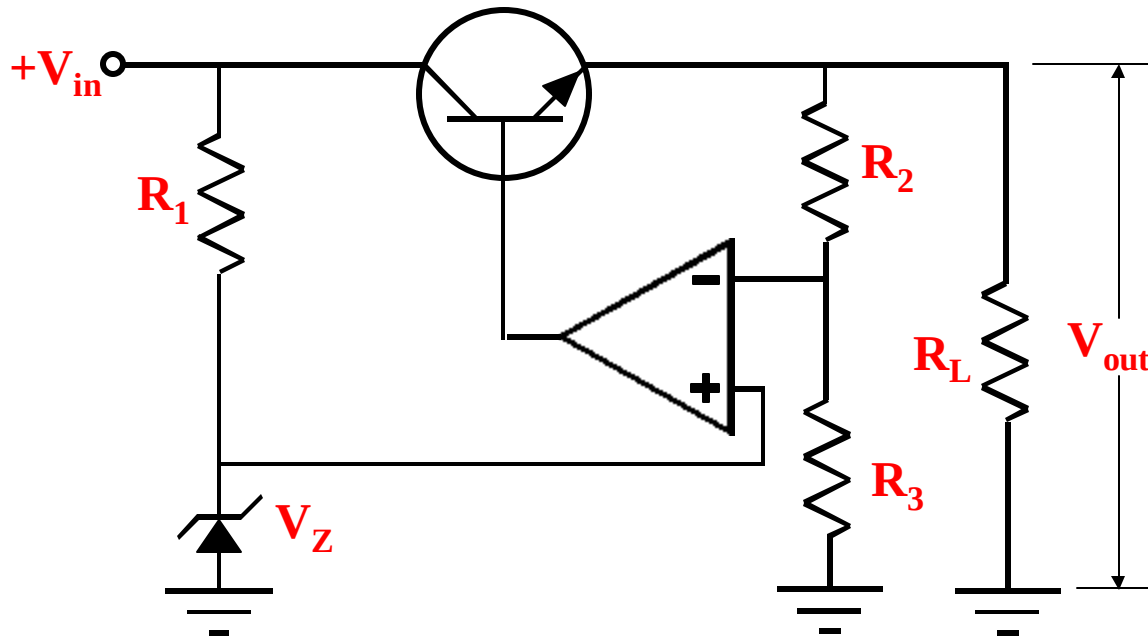

Disipación de potencia y eficiencia

❑ Ver: Fuentes Reguladas - Especificaciones y Disipación de Potencia del Transistor de Paso

❑ Eficiencia = $\frac{V_{OUT}}{V_{IN}} \times 100\%$

❑ Disipación de potencia en el transistor de paso

$$P_{Q1} = V_{CE} I_C$$

$$V_{CE} = V_{ent} - V_{sal}$$

$$I_C = I_L \text{ (corriente de carga)}$$

❑ Potencia máxima

$$V_{ent} = V_{ent_{max}}$$


$$I_L = I_{L_{max}}$$

$$P_{Q1_{max}} = (V_{ent_{max}} - V_{sal}) I_{L_{max}}$$

Especificaciones del transistor de paso

❑ Condiciones de carga normales

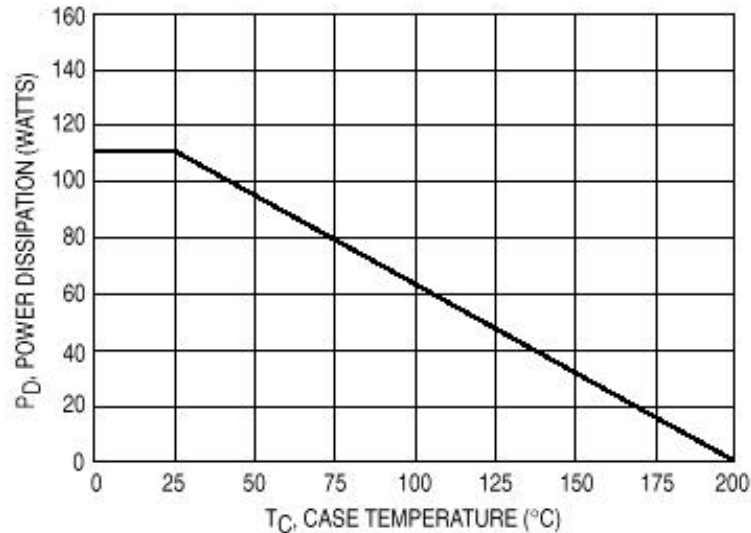- ❑ $I_{Cmax} > I_{Lmax}$
- ❑ $V_{CEOmax} > V_{entmax}$
- ❑ $h_{FEmin} > I_{Lmax}/I_{Bmin}$
- ❑ $P_{Dmax} > P_{Q1max}$



Disipadores y transistores de potencia

❑ Encapsulados



CASE 221A
(TO-220AB)



CASE 1-07
TO-204AA
(TO-3)

❑ Resistencia térmica

$$R_q [^{\circ}\text{C}/\text{W}] = \Delta T / \text{Pot}$$

$$\Delta T = T_j - T_A$$


$$R_{qTotal} = R_{qjc} + R_{qcd} + R_{qda}$$

$$T_j = T_A + (R_{qjc} + R_{qcd} + R_{qda}) \text{Pot}$$


Cálculo:

$$R_{qda} = (T_j - T_A) / \text{Pot} - R_{qjc} - R_{qcd}$$


Disipadores y transistores de potencia

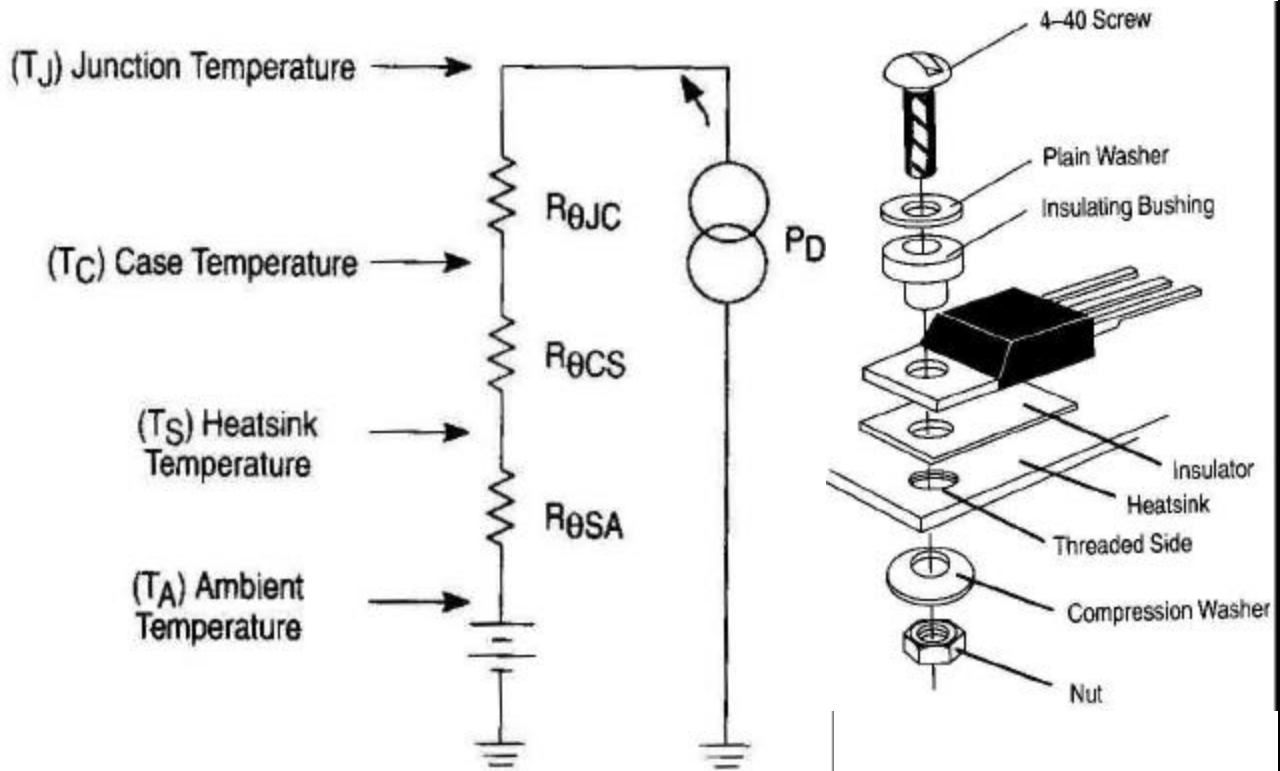


Regulador con limitación de corriente

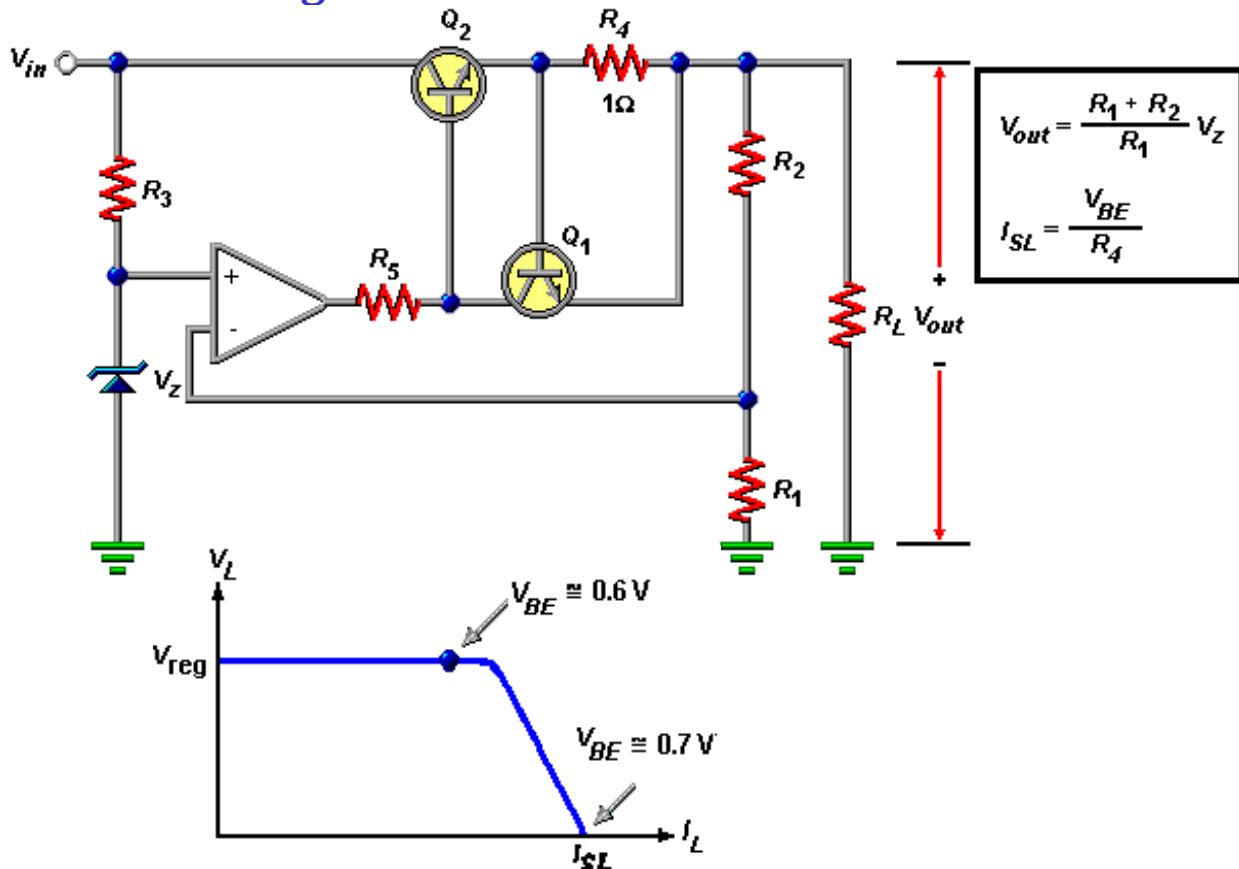

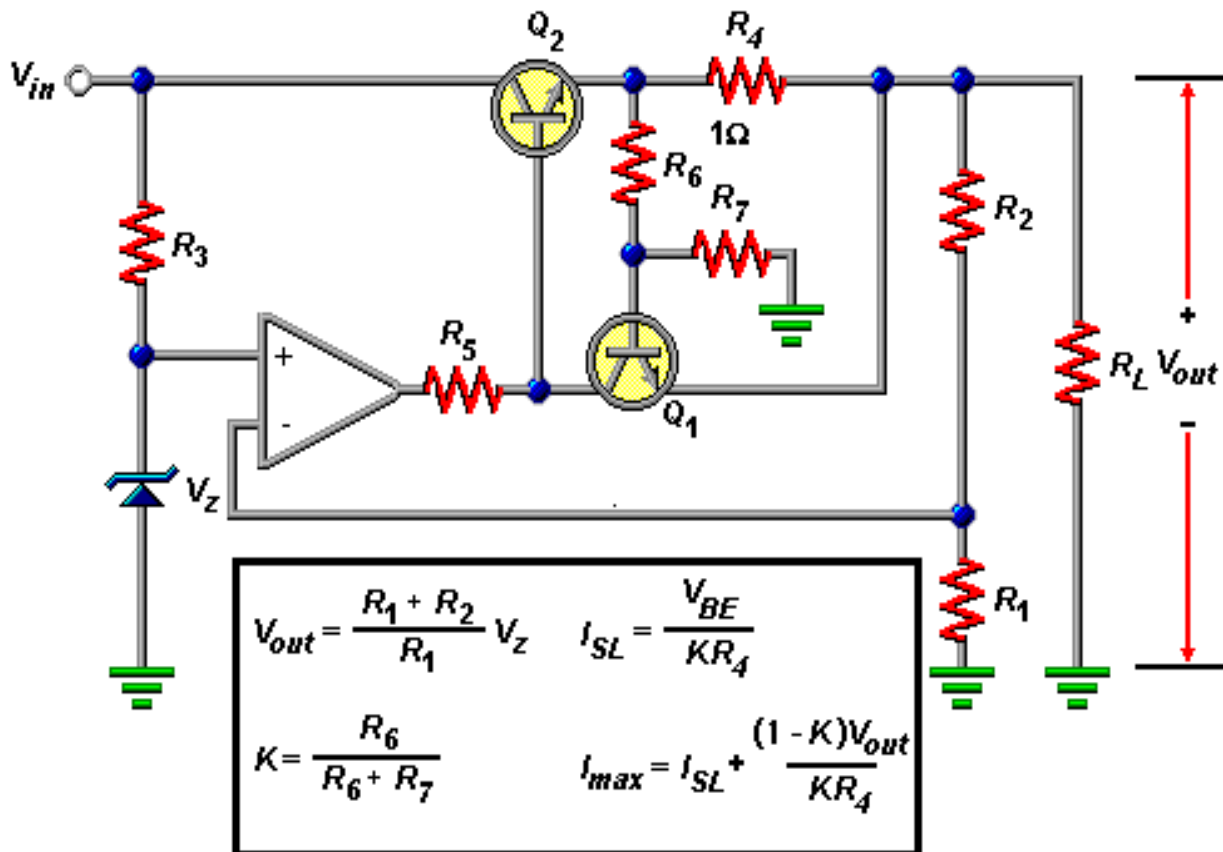
Limitación de corriente de corte plegado (Foldback)



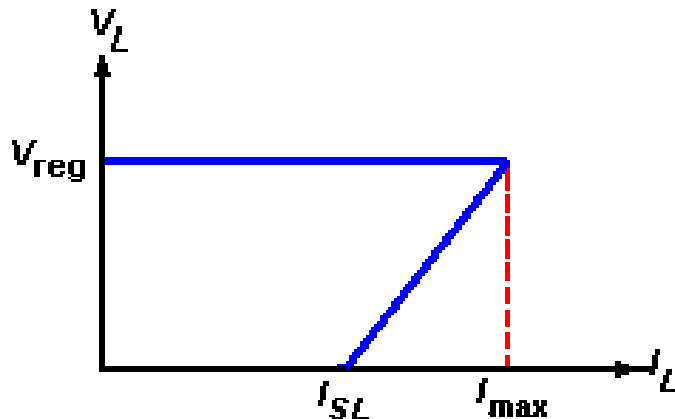Limitación de corriente de corte plegado (Foldback)



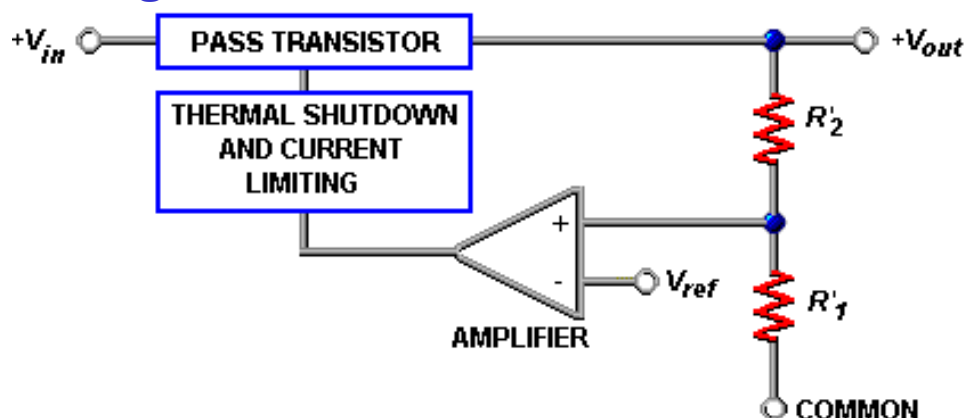
Reguladores lineales en C.I. de tres terminales




❑ Reguladores fijos

❑ Serie 78XX

❑ Serie 79XX

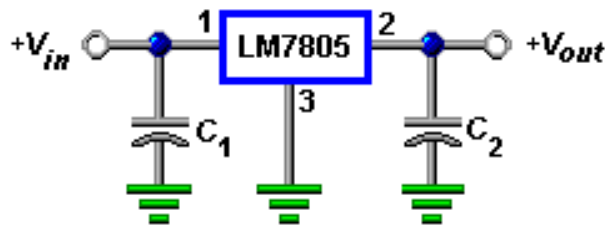

❑ Fuentes duales

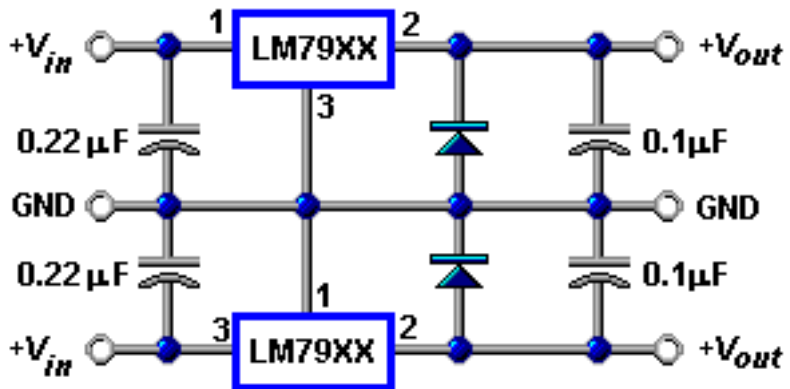

❑ Reguladores ajustables

❑ LM317

❑ Tensión de salida


$$V_{OUT} = \frac{R_1 + R_2}{R_1} V_{REF} + I_{ADJ} R_2$$

$$V_{REF} = 1.25V$$


$$R_1 \leq 240\Omega \Rightarrow I_{REF} > I_{ADJ}$$

$$V_{OUT} = \frac{R_1 + R_2}{R_1} (1.25V)$$

❑ Rechazo al rizado

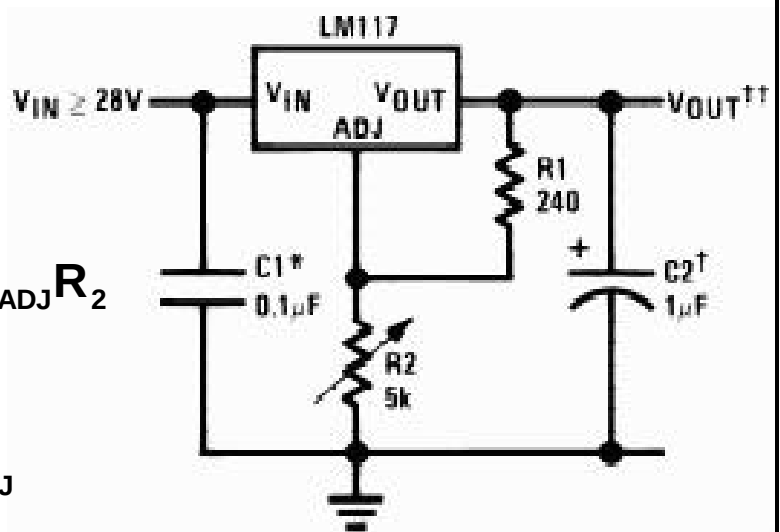

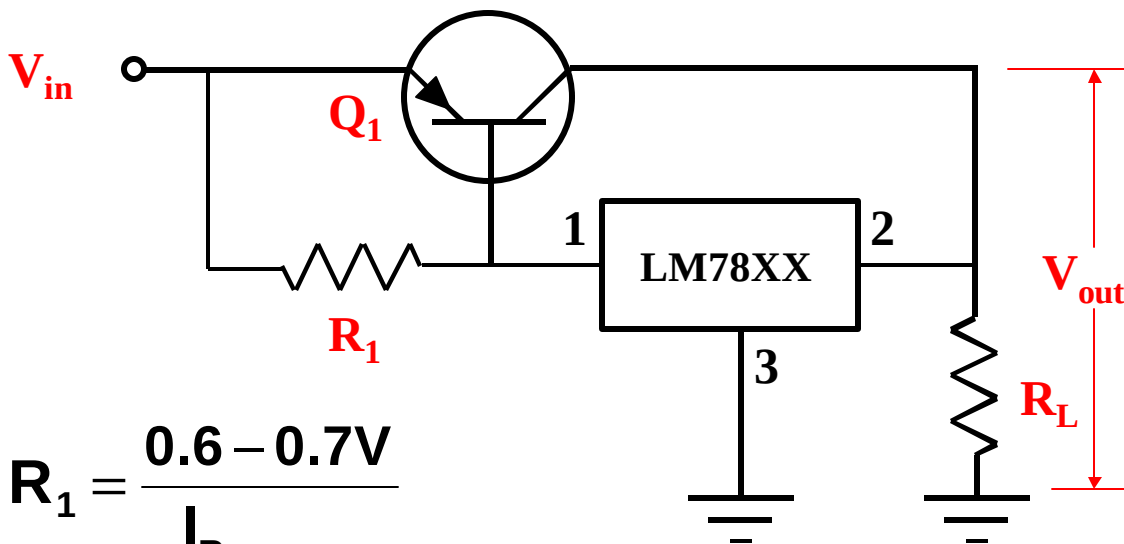Regulador integrado con amplificador de corriente




$$R_1 = \frac{0.6 - 0.7V}{I_{\text{Reg.max}}}$$

$$I_{\text{Reg.max}} > \frac{I_{L.\text{max}}}{h_{FE\text{MIN}}}$$

$$V_{\text{in}} \geq V_{\text{DROPOUT}} + 0.7V$$

Con limitación de corriente

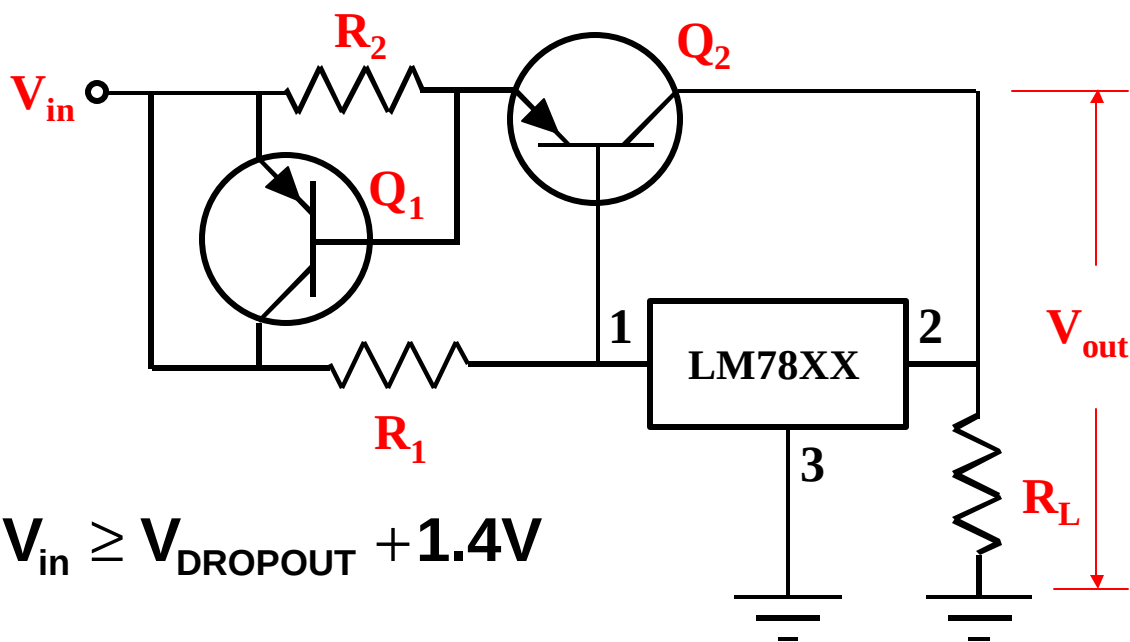

$$V_{\text{in}} \geq V_{\text{DROPOUT}} + 1.4V$$